

Appendix A: Low Pass Filter Design

(for a detailed Tutorial see https://www.electronics-tutorials.ws/filter/filter_2.html)

The simple RC low-pass filter of Figure 3 works like a voltage divider. **The “resistance” of a capacitor depends inversely on frequency** and is referred to as *reactance*,

$$Z_c = \frac{1}{2\pi fC}.$$

Considering the RC circuit as a voltage divider:

$$V_{out} = V_{in} \frac{Z_c}{R+Z_c} \quad (\text{for EE's it should be } |V_{out}| = |V_{in}| \frac{|Z_c|}{|R+Z_c|})$$

Point is, as Z_c gets smaller V_{out} gets smaller. Since Z_c gets smaller as frequency goes up, V_{out} gets smaller as frequency goes up. It's useful to determine the frequency where $V_{out} = V_{in}/2$. We call this the “cutoff” frequency.

Solving:

$$F_{CO} = \frac{1}{2\pi RC}$$

The RC circuit “passes through” frequencies below F_{CO} and “blocks” frequencies above F_{CO} .

Example:

We want to cut off frequencies above 1000Hz and $R = 1000$ Ohms, find C .

Solution:

$$F_{CO} = 1000\text{Hz} = \frac{1}{2\pi RC}, \quad C = \frac{1}{2\pi 10^6} = 1.6 \times 10^{-7} \text{ Farads} = 0.16\mu F$$